

Choose tail current  $75 \mu A$

Current through diff part:  $37.5 \mu A$

To start with

$$\text{Take } (V_{gs} - V_{th})_{M4} = 0.1 V.$$

$$V_{th} = 0.37$$

$$V_g = 0.9 V$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right)_4 \cdot (V_{gs} - V_{th})^2$$

$$37.5 = \frac{1}{2} \times 230 \cdot \left(\frac{W}{L}\right)_4 \times (0.1)^2$$

$$\boxed{\left(\frac{W}{L}\right)_4 = 32.}$$

for pmos,

$$37.5 = \frac{1}{2} \times 100 \cdot \left(\frac{W}{L}\right)_2 \times (0.1)^2$$

$$\boxed{\left(\frac{W}{L}\right)_2 = 75}$$

(Later changed to 55 to maintain decent gain in 2nd stage)

$$\text{Current through } M6 = \frac{75}{10} = 7.5 \mu A$$

$$\text{Choose } \boxed{\left(\frac{W}{L}\right)_6 = 4.}$$

$$\boxed{\left(\frac{W}{L}\right)_5 = 40.}$$

Gain Calculation, (Theoretical,

$$V_{gs} - V_{thn} = 0.1$$

$$A_{V,FE} \therefore g_m = \frac{2 I_D}{0.1} \quad (\lambda's \text{ of both are equal})$$

$$R_{out} = r_{ON} \parallel r_{OP} = \frac{1}{2 \lambda I_D} \quad (\text{from DC log file})$$

$$\text{Taking } \lambda \approx 0.1 \quad (\text{from DC-log file})$$

$$A_v = g_m \cdot R_{out} \approx 100$$

$$\text{Simulated gain (Stage 1) in LTSpice} \\ = 80$$

$$A_v = \left( \frac{W}{L} \right) \cdot 0.88 \cdot \frac{1}{2} = 80$$

~~V<sub>ds</sub> =~~

for pmos M2,

$$V_{sg} = 0.1 + V_{tp}$$

$$1.8 - V_g = 0.1 + V_{tp}$$

$$V_g = 1.7 - 0.39$$

$$V_g \approx 1.31$$

$$V_{d1}$$

$$A = \left( \frac{W}{L} \right)$$

$$A_{OP} = \left( \frac{W}{L} \right)$$

## 2nd Stage design

Choose  $I_D = 30 \mu A$   $\therefore \left(\frac{W}{L}\right)_8 = \frac{15}{7.5} \times 30$

$$(V_{gs} - V_{tp}) = 0.1 V$$

$$\boxed{\left(\frac{W}{L}\right)_8 = 16}$$

$$\therefore \boxed{\left(\frac{W}{L}\right)_7 = 60}$$

→ Taken as 19  
to get decent gain

Note: Due to variation in  $V_{tp}$  in simulation

it is changed to 19 to get decent gain,

in simulation actual  $V_{gs} - V_{tp} \approx 0.5 V$ .

~~three~~

~~to~~

~~Calculated~~ bias data,

	M <sub>1</sub>	M <sub>2</sub>	M <sub>3</sub>	M <sub>4</sub>	M <sub>5</sub>	M <sub>6</sub>	M <sub>7</sub>	M <sub>8</sub>
$ V_{gs} - V_{th}  (V)$	0.14	0.14	0.08	0.08	<del>0.12</del> 0.12	0.12	0.052	0.053
$g_m (\mu A V^{-1})$	442	442	612	612	1030	108	415	406
$r_o (M\Omega)$	0.29	0.29	<del>0.26</del>	0.26	10	0.01	<del>0.01</del> 7.7	0.11
$I_D (\mu A)$	35	35	35	35	70	7.5	23	23
$W$	55	55	32	32	40	4	16	35
$L (\mu)$	1	1	<del>1</del>	1	1	1	0.18	0.18